
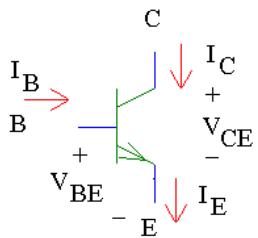


DC Bipolar Transistor Models - Jaeger


n-p-n

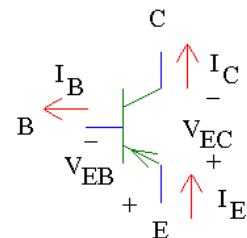


p-n-p



Cut-Off:

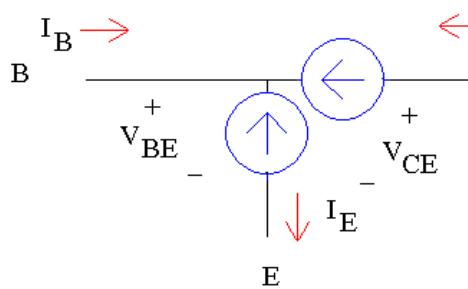

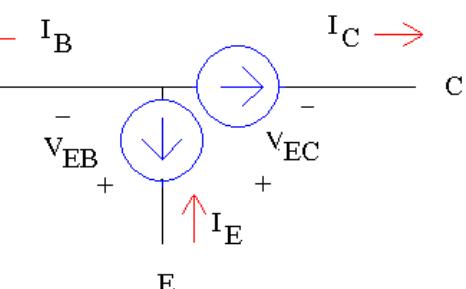$I_E \approx I_C \approx I_B \approx 0\text{mA}$




$$V_{BE} < -4kT/q \quad V_{BC} < -4kT/q$$

$$I_C = I_S/\beta_R \quad I_E = -I_S/\beta_F \quad I_B = -I_S/\beta_F - I_S/\beta_R$$

$$V_{EB} < -4kT/q \quad V_{CB} < -4kT/q$$

Forward Active:

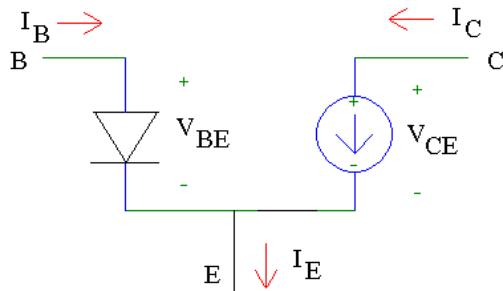

$$V_{BE} = (q/kT)\ln I_S$$

$$V_{BE} > 4kT/q$$

$$I_B = (I_S/\beta_F)[\exp(V_{BE}/V_T) - 1] - (I_S/\beta_R)$$


$$I_B \approx (I_S/\beta_F) \exp(V_{BE}/V_T)$$

$$I_C = I_S[\exp(V_{BE}/V_T) + 1/\beta_R]$$

$$I_C \approx I_S \exp(V_{BE}/V_T)$$

$$I_E = I_S [(1/\alpha_F)(\exp(V_{BE}/V_T) + 1/\beta_R)]$$
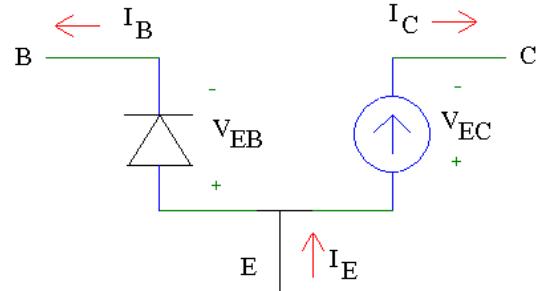
$$I_E \approx (I_S/\alpha_F) \exp(V_{BE}/V_T)$$



$$V_{EB} = (q/kT)\ln I_S$$

$$V_{EB} > 4kT/q$$

$$I_B = (I_S/\beta_F)[\exp(V_{EB}/V_T) - 1] - (I_S/\beta_R)$$

$$I_B \approx (I_S/\beta_F) \exp(V_{EB}/V_T)$$

$$I_C = I_S[\exp(V_{EB}/V_T) + 1/\beta_R]$$

$$I_C \approx I_S \exp(V_{EB}/V_T)$$

$$I_E = I_S [(1/\alpha_F)(\exp(V_{EB}/V_T) + 1/\beta_R)]$$


$$I_E \approx (I_S/\alpha_F) \exp(V_{EB}/V_T)$$

Saturation:

$$I_B = (I_S/\beta_F) \exp(V_{BE}/V_T) + (I_S/\beta_R) \exp(V_{CE}/V_T) \approx (I_S/\beta_F) \exp(V_{BE}/V_T)$$


$$I_C = I_S [\exp(V_{BE}/V_T) + 1/\beta_R] \approx I_S \exp(V_{BE}/V_T)$$
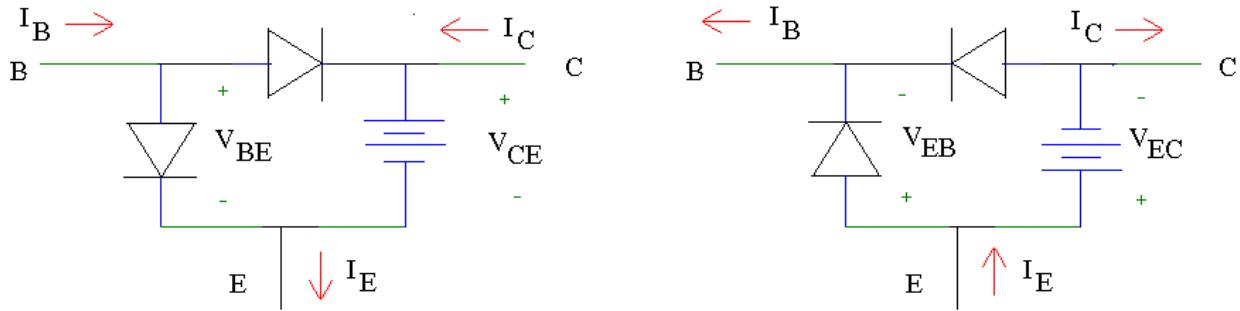
$$I_E = I_S [(1/\alpha_F)(\exp(V_{BE}/V_T) + 1/\beta_R)] \approx (I_S/\alpha_F) \exp(V_{BE}/V_T)$$



Reverse Active:

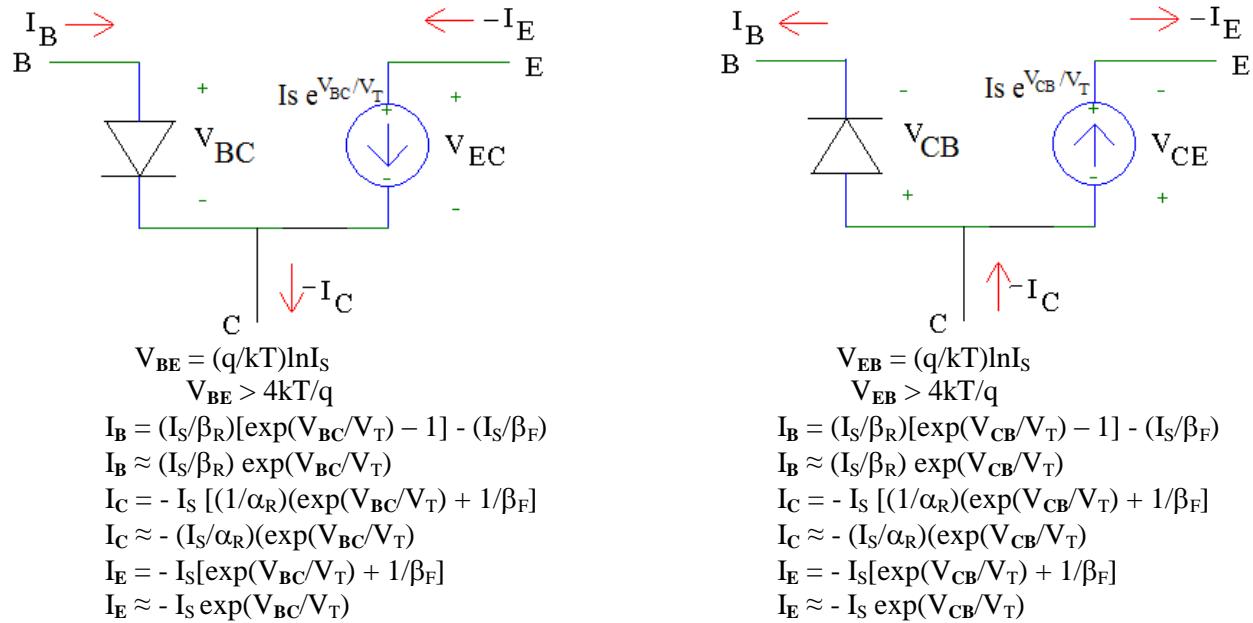
$$I_E = \beta_R I_B, I_C = (\beta_R + 1) I_B$$



Further Simplification of DC Bipolar Transistor Models – Jaeger

Cut-Off:

$$I_E = I_C = I_B = 0 \text{ mA}$$

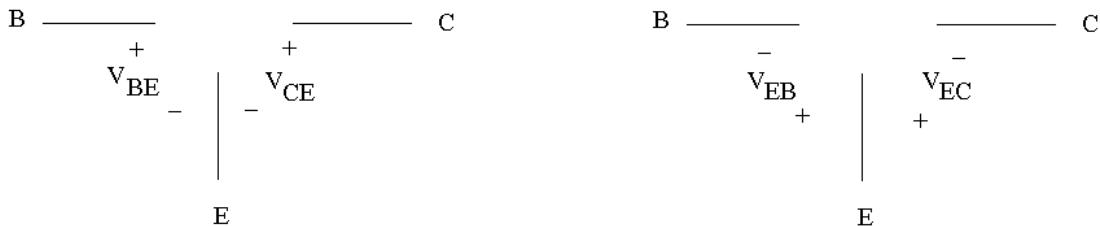



$$V_{BE} < V_{on} \text{ (base-emitter diode)}$$

$$V_{EB} < V_{on} \text{ (base-emitter diode)}$$

Saturation:

$$I_C \sim I_{SC}$$

$$I_C < \beta_F I_B$$

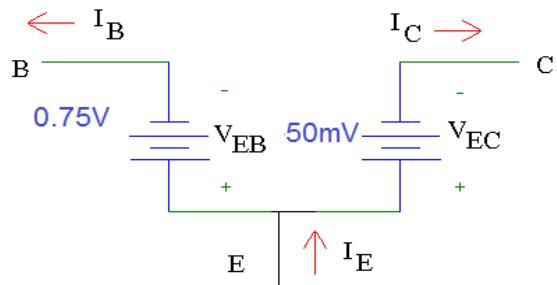
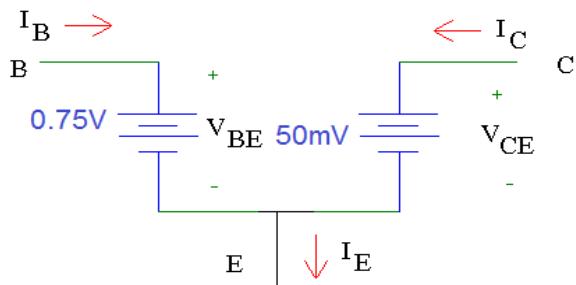


$$V_{BE} = 0.75V \quad V_{CE} = 50mV$$

$$V_{EB} = 0.75V \quad V_{EC} = 50mV$$

Forward Active:
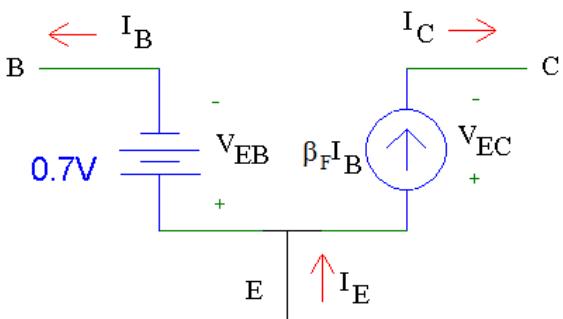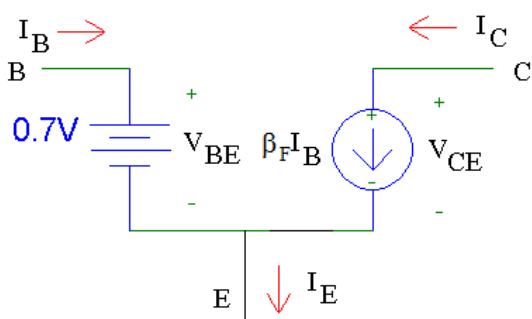
$$I_C = \beta_F I_B, \quad I_E = (\beta_F + 1) I_B$$





$$V_{BE} = 0.7V \quad V_{CE} > 50mV$$

$$V_{EB} = 0.7V \quad V_{EC} > 50mV$$

Reverse Active:
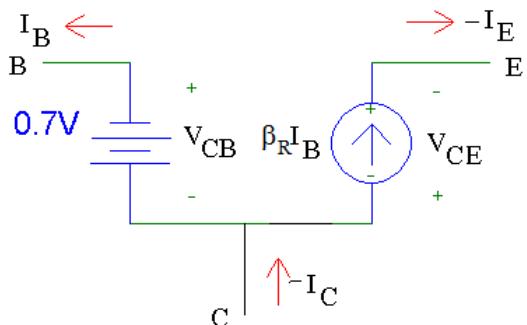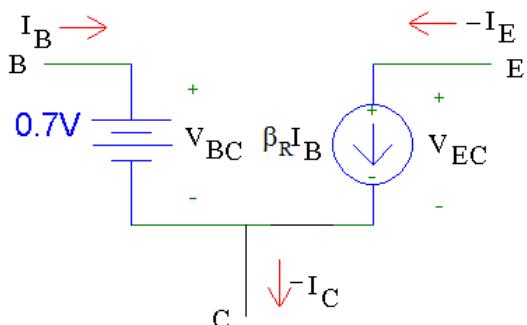
$$I_E = \beta_R I_B, \quad I_C = (\beta_R + 1) I_B$$



$$V_{BC} = 0.7V \quad V_{EC} > 50mV$$

$$V_{CB} = 0.7V \quad V_{CE} > 50mV$$